
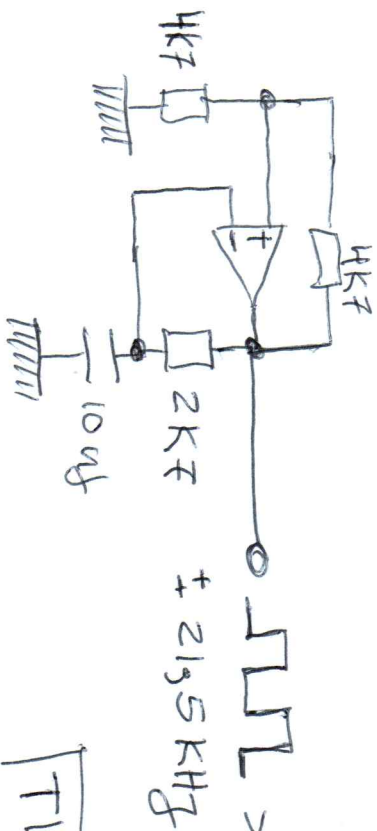



Sergio Sanchez
1020881

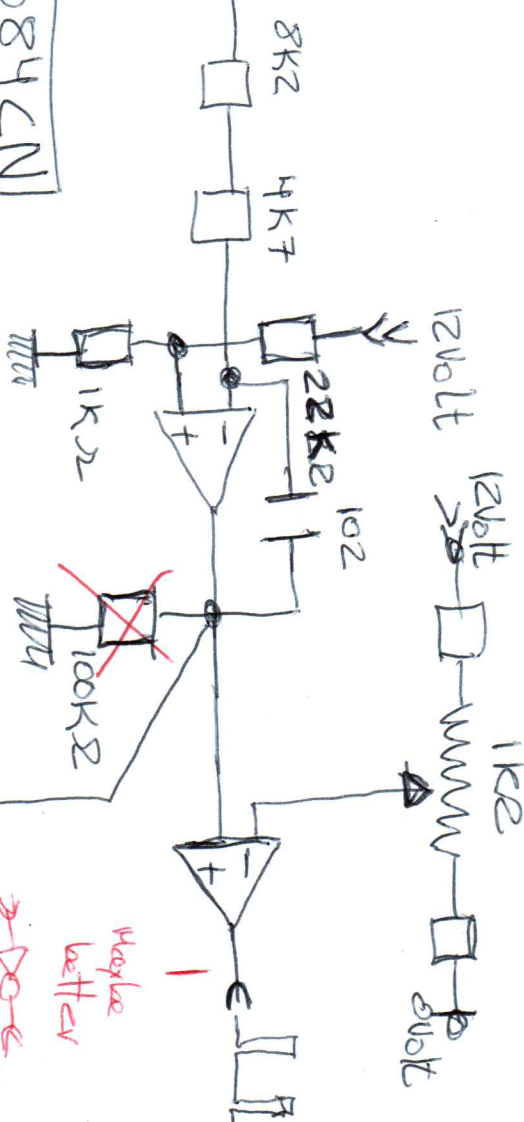

TL084CN
14 pin



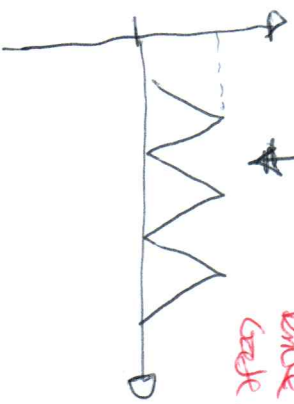Maybe better
for
Schmitt
trigger
circuit.



$$f_{osc} = \frac{1}{4RC}$$